




Low Dropout Regulators

Pavan Kumar Hanumolu
University of Illinois, Urbana-Champaign


Updated Slides: <https://uofi.box.com/CICC15-LDO>

Role of a Low Dropout Regulator

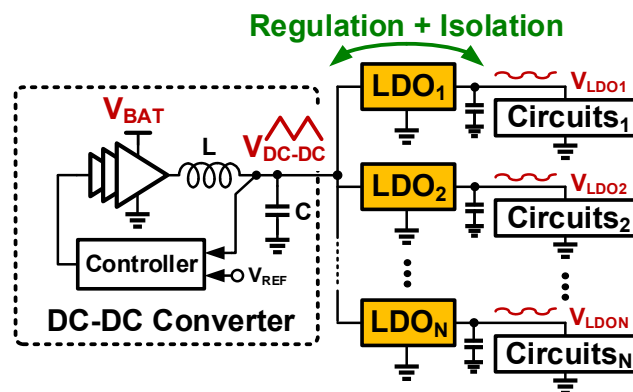

- ❑ Ripple suppression
- ❑ Isolation
- ❑ Low noise


Conceptual LDO Regulator Implementation

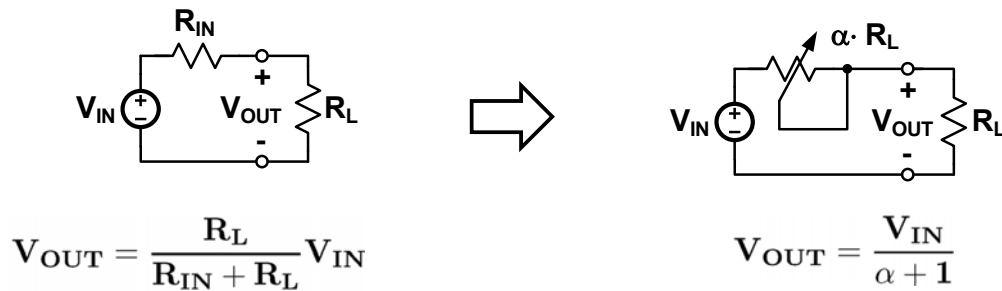

- ❑ Output voltage generated using a resistive divider
 - Fixed divide ratio → sensitive to load current changes

- ❑ Feedback loop regulates R_{IN} such that it is always a desired fraction of load current
 - Output voltage is independent of load current


Conceptual LDO Regulator Implementation

 

- ❑ Feedback adjusts R_{IN} such that $V_{OUT} = V_{REF}$
 - Ideally independent of V_{IN}


- ❑ Output capacitor (C_O) used to “filter” ripple/noise

LDO Block Diagram

 

- ❑ Bandgap circuit provides fixed reference voltage
- ❑ Feedback resistors used to level shift output voltage
 - Output voltage can be varied by changing R_{F2}
- ❑ Variable resistor is implemented using "pass device"
 - Usually NMOS or PMOS

LDO Block Diagram

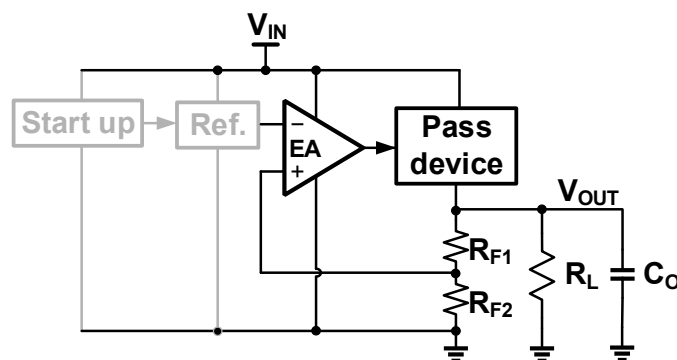


- ❑ Bandgap circuit provides fixed reference voltage
- ❑ Feedback resistors used to level shift output voltage
 - Output voltage can be varied by changing R_{F2}
- ❑ Variable resistor is implemented using "pass device"
 - Usually NMOS or PMOS

❑ This tutorial: **Regulation loop design**


Tutorial Roadmap

- ❑ Performance metrics
- ❑ Stability
- ❑ Power supply rejection
- ❑ Summary

Performance Metrics

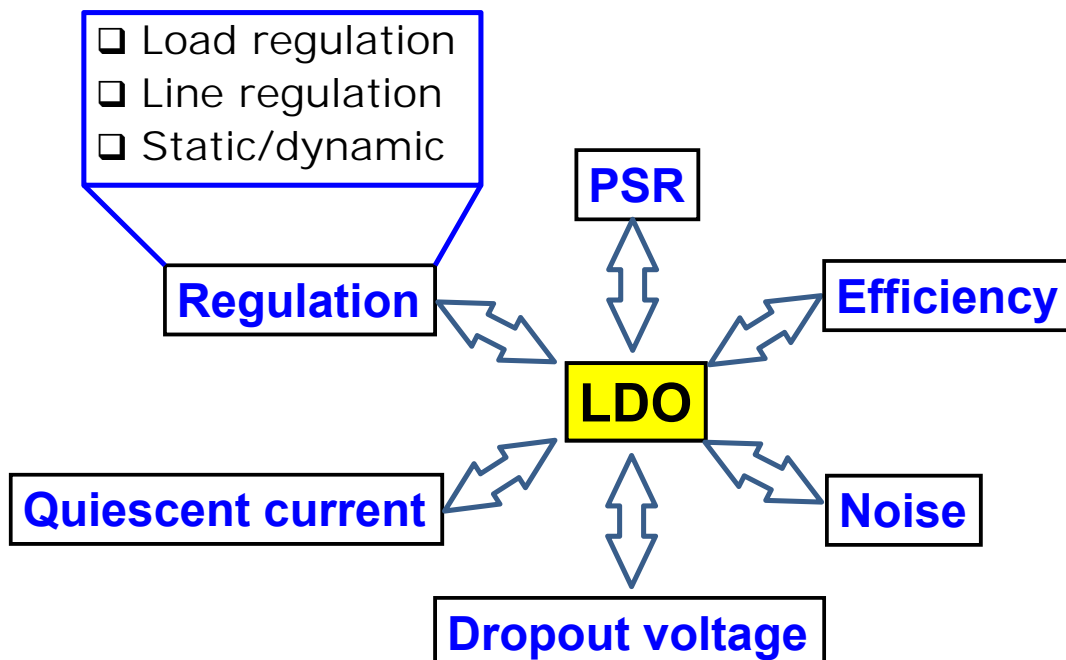


Dropout Voltage

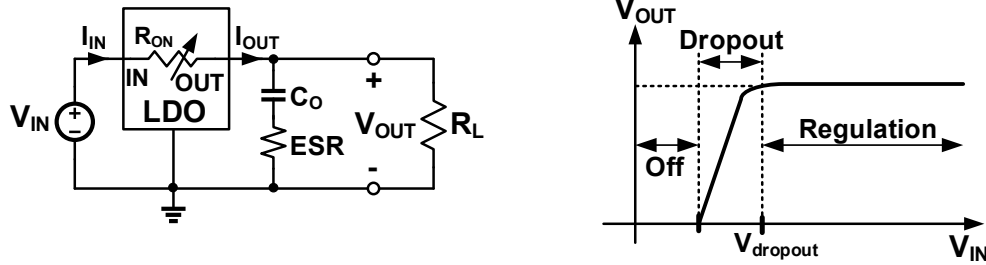

- ❑ $V_{IN} - V_{OUT}$ at which V_{OUT} is no longer regulated
- ❑ Dropout voltage depends on pass device/load current
- ❑ Dropout voltage is in the range of 0.1 to 0.5V

Quiescent Current

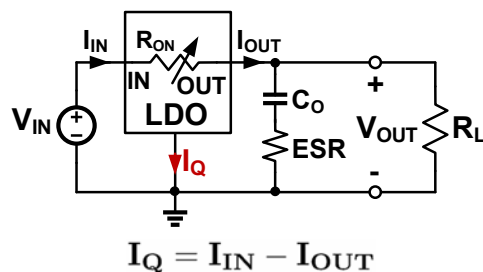

- ❑ I_Q is mainly due to bias currents in:
 - Reference generator
 - Error amplifier
 - Feedback resistors
 - Support circuits
- ❑ I_Q is almost independent of load current

Efficiency

$$\text{Current efficiency : } \eta_I = \frac{I_{OUT}}{I_{IN}} \times 100$$

$$\eta_I = \frac{I_{OUT}}{I_{OUT} + I_Q} \times 100$$

Efficiency

$$\text{Current efficiency : } \eta_I = \frac{I_{OUT}}{I_{IN}} \times 100$$

$$\eta_I = \frac{I_{OUT}}{I_{OUT} + I_Q} \times 100$$

$$\text{Power efficiency : } \eta = \frac{I_{OUT} V_{OUT}}{(I_{OUT} + I_Q) V_{IN}} \times 100 \approx \frac{V_{OUT}}{V_{IN}} \times 100$$


Example:

$$V_{OUT} = 1.8 \text{ V}, \quad V_{IN} = 2.5 \text{ V}, \quad I_{OUT} = 25 \text{ mA}, \quad I_Q = 50 \mu\text{A}$$

$$\begin{aligned} \Rightarrow \eta_I &= 99.8\% \\ \eta &= 71.86\% \end{aligned}$$

Line Regulation

 - Measure of LDO's ability to maintain desired V_{OUT} with varying V_{IN} (static metric)




$$\text{Line regulation } L_R = \frac{\Delta V_{OUT}}{\Delta V_{IN}}$$

$$\Delta V_{LR} = \Delta V_{IN} \times \text{Line regulation}$$

$$\Delta V_{LR} = [\text{mV/V}] @ \Delta V_{IN} = V_1$$

Load Regulation

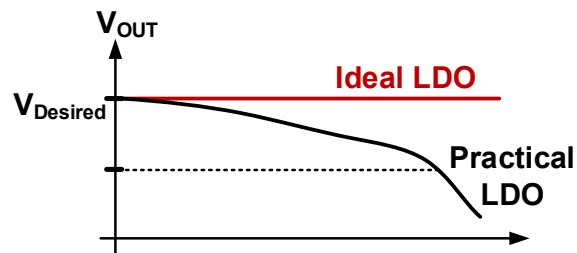- Measure of LDO's ability to maintain desired V_{OUT} with varying I_{OUT}




$$\text{Load regulation} = \frac{\Delta V_{OUT}}{\Delta I_{OUT}}$$

$$\Delta V_{LDR} = \Delta I_{OUT} \times \text{Output resistance}$$


Line Transient Response

 - Measure of LDO's ability to maintain desired V_{OUT} with varying V_{IN} (dynamic metric)





Load Transient Response

 - Measure of LDO's ability to maintain desired V_{OUT} with varying I_{OUT} (dynamic metric)



Power Supply Rejection

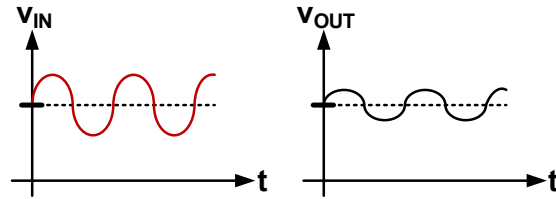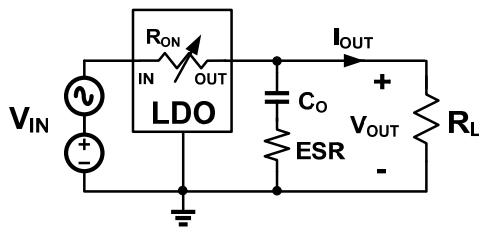- ❑ Regulator's ability to reject V_{OUT} variations due to changes in V_{IN}



$$\text{PSR}(f) = \frac{\Delta V_{OUT}(f)}{\Delta V_{IN}(f)}$$

- ❑ Similar to line regulation BUT measured vs. frequency
- ❑ Similar to line transient BUT measured for “small signal” variations



Accuracy

- ❑ Includes all non-ideal effects:
 1. Line/load regulation
 2. Reference voltage drift
 3. Error amplifier offset drift
 4. Feedback resistor tolerance



$$\text{Accuracy} \approx |\Delta V_{LR}| + |\Delta V_{LDR}| + \sqrt{\Delta V_{O,REF}^2 + \Delta V_{O,EA}^2 + \Delta V_R^2}$$

LDO Types


Pass device: PMOS or NMOS

 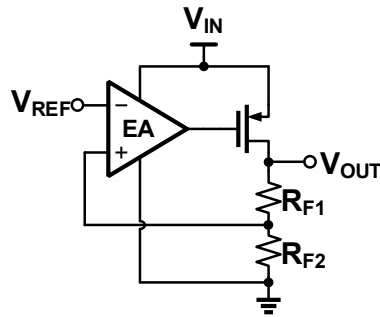

Cap or Cap-less LDOs

 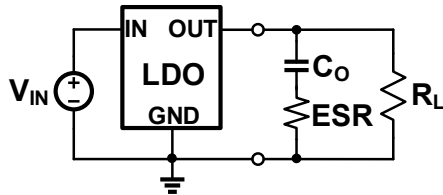



PMOS LDO w/ Output Capacitor^[1]

 

$$V_{OUT} = V_{REF} \left[1 + \frac{R_{F1}}{R_{F2}} \right]$$

- ❑ PMOS pass device
 - Dropout voltage is approximately V_{DSAT} (0.1-0.4V)
- ❑ Output capacitor C_O placed off chip
 - Comes with ESR

Output Voltage Calculation

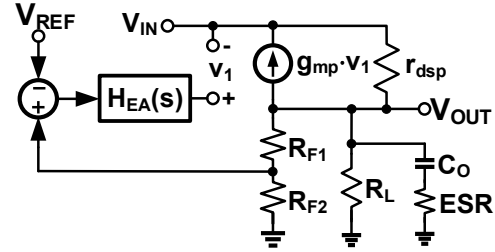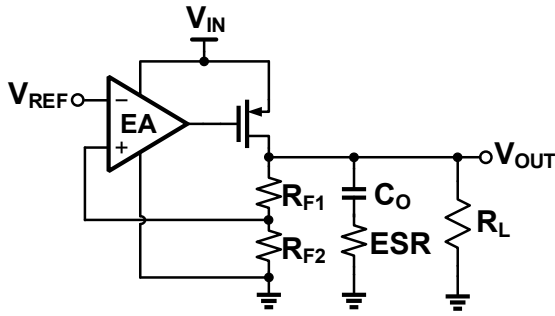


□ Use KCL/KVL to calculate transfer functions

$$H_{IN} = \frac{V_{OUT}}{V_{IN}} \quad H_{REF} = \frac{V_{OUT}}{V_{REF}}$$

$$V_{OUT} = H_{IN} V_{IN} + H_{REF} V_{REF}$$

Signal Flow Representation

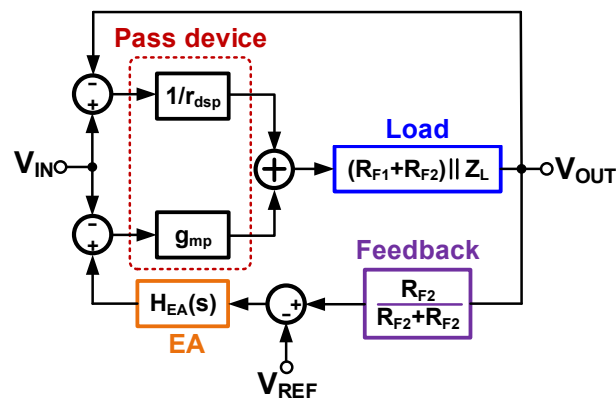

$$Z_L = R_L \parallel \left(\frac{1}{sC_O} + R_{ESR} \right)$$

$$@ \text{ DC } Z_L = R_L \quad H_{EA}(s) = A_{EA0} \quad (R_{F1} + R_{F2}) \parallel R_L = R_{FL}$$

□ Use Mason's gain rule to find transfer functions

Mason's Gain Rule

$$H = \frac{\sum_j M_j \Delta_j}{\Delta}$$

H = transfer function of the system

j = index number of a forward path from input to output

M_j = gain of forward path j from input to output

Δ = $1 - \sum$ (all loop gains)


+ \sum (nontouching loop gains multiplied two at a time)

- \sum (nontouching loop gains multiplied three at a time)

+ \sum (nontouching loop gains multiplied four at a time)...

Δ_j = Δ calculated after excluding all feedback loops that intersect with forward path j

Mason's Gain Rule: Example

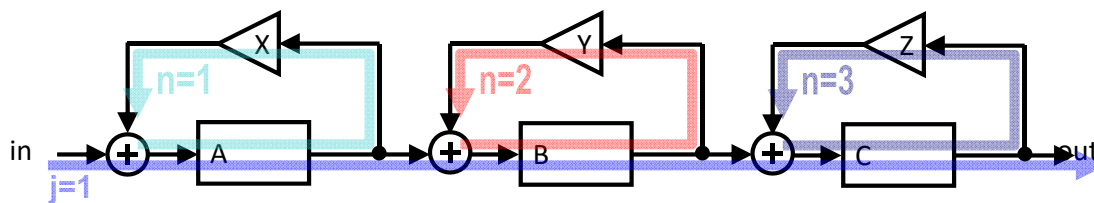


$$H = \frac{\sum_j M_j \Delta_j}{\Delta}$$

- $M_1 = ABC$
- $\Delta_1 = 1$
- $\Delta = 1 - (L_1 + L_2 + L_3) + (L_1 L_2 + L_2 L_3 + L_3 L_1) - (L_1 L_2 L_3)$
 $= 1 - (AX + BY + CZ) + (AXBY + BYCZ + CZAX) - (AXBYCZ)$

$$H = \frac{ABC}{1 - (AX + BY + CZ) + (AXBY + BYCZ + CZAX) - (AXBYCZ)}$$

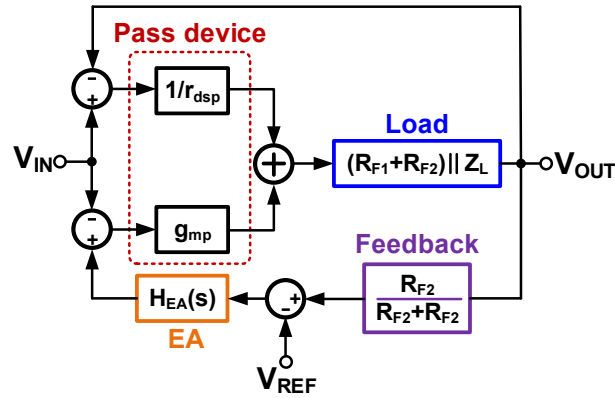Output Voltage Calculation (due to V_{REF})




$$\frac{V_{OUT}}{V_{REF}} = \frac{A_{EA0} \cdot g_{mp} \cdot R_{FL}}{1 + A_{EA0} \cdot g_{mp} \cdot R_{FL} \cdot \beta + R_{FL} / r_{dsp}}$$

$$\frac{V_{OUT}}{V_{REF}} = \frac{A_{EA0} \cdot g_{mp} \cdot r_{dsp}}{1 + A_{EA0} \cdot g_{mp} \cdot r_{dsp} \cdot \beta + r_{dsp} / R_{FL}}$$

$$\approx \frac{1}{\beta} \text{ if } A_{EA0} \cdot g_{mp} \cdot R_{FL} \cdot \beta \gg 1$$

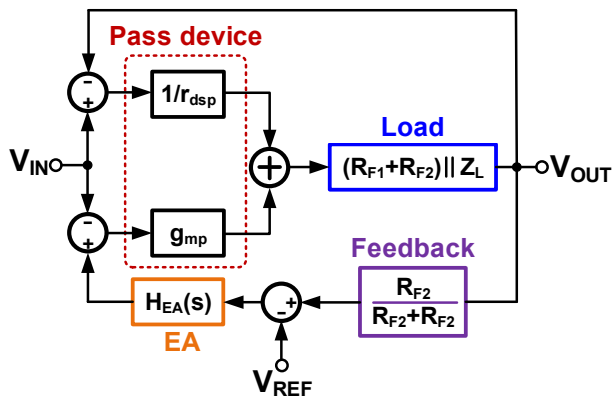Output Voltage Calculation (due to V_{IN})



$$\beta = \frac{R_{F2}}{R_{F1} + R_{F2}}$$

$$@ \text{ DC } Z_L = R_L$$

$$H_{EA}(s) = A_{EA0}$$

$$(R_{F1} + R_{F2}) || R_L = R_{FL}$$

$$\frac{V_{OUT}}{V_{IN}} = \frac{g_{mp} \cdot R_{FL} + 1 / r_{dsp} R_{FL}}{1 + A_{EA0} \cdot g_{mp} \cdot R_{FL} \cdot \beta + \frac{R_{FL}}{r_{dsp}}}$$

$$\frac{V_{OUT}}{V_{IN}} = \frac{1 + g_{mp} r_{dsp}}{1 + \left(A_{EA0} \cdot g_{mp} \cdot r_{dsp} \beta + \frac{r_{dsp}}{R_{FL}} \right)}$$

$$\frac{V_{OUT}}{V_{IN}} \approx \frac{1}{A_{EA0} \cdot \beta} \text{ if } g_{mp} r_{dsp} \gg 1$$

Line Regulation


$$L_R = \frac{\Delta V_{OUT}}{\Delta V_{IN}} = \frac{1 + g_{mp}r_{dsp}}{1 + A_{EA0} \cdot g_{mp} \cdot r_{dsp} \cdot \beta}$$

$$\Rightarrow L_R \approx \frac{1}{\beta A_{EA0}}$$

$$\Delta V_{OUT} = \frac{\Delta V_{IN}}{\beta A_{EA0}} + \frac{(\Delta V_{REF} + \Delta V_{OS})}{\beta}$$

- ❑ Changes in V_{IN} suppressed by error amp. gain
- ❑ Reference and offset voltage drift amplified by feedback factor

Load Regulation

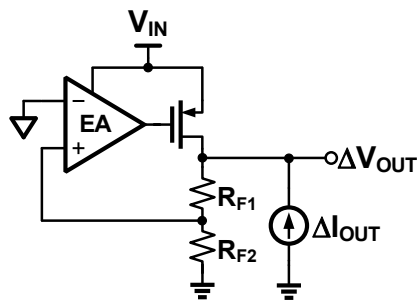


$$L_{DR} = \frac{\Delta V_{OUT}}{\Delta I_{OUT}}$$

$$\Delta I_{OUT} = \frac{\Delta V_{OUT}}{[r_{dsp} || (R_{F1} + R_{F2})]} + \Delta V_{OUT} \cdot \beta \cdot A_{EA0} \cdot g_{mp}$$

$$\Rightarrow L_{DR} \approx \frac{r_{dsp} || (R_{F1} + R_{F2})}{1 + \beta A_{EA0} \cdot g_{mp} \cdot [r_{dsp} || (R_{F1} + R_{F2})]} \approx \frac{r_{dsp}}{1 + T_0}$$


- ❑ Output impedance lowered by loop gain

Stability

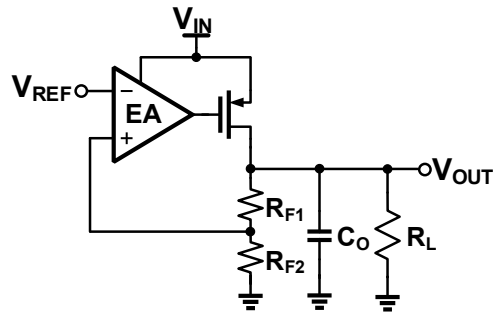

- ❑ Closely-spaced poles compromise stability
- ❑ Needs frequency compensation
 - Pole-zero “cancellation”
 - Pole splitting

Loop Gain

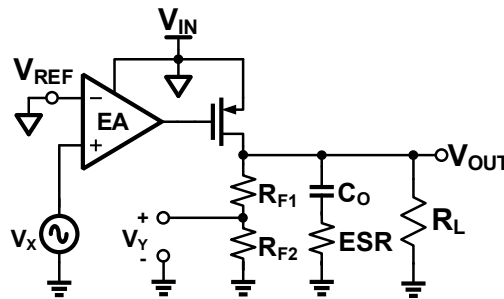


$$\text{Loop gain } T(s) = \frac{-V_Y}{V_X} = H_{EA}(s) \cdot g_{mp} \cdot [r_{dsp} \parallel (R_{F1} + R_{F2}) \parallel Z_L] \cdot \beta$$

$$= A_{EA0} \cdot g_{mp} \cdot [r_{dsp} \parallel (R_{F1} + R_{F2})] \cdot \beta$$

$$\text{DC loop gain } T_0 \approx A_{EA0} \cdot g_{mp} \cdot r_{dsp} \cdot \beta$$

Loop Gain Transfer Function

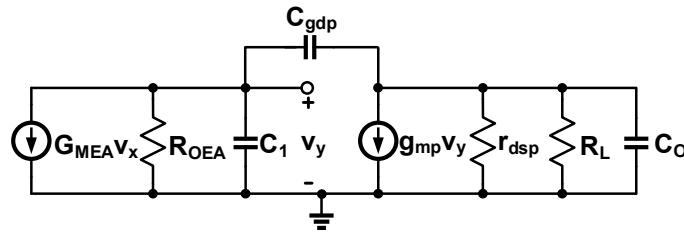


$$T(s) = \frac{-v_y(s)}{v_x(s)} = \frac{\beta G_{MEA} \cdot R_{OEA} \cdot g_{mp} \cdot R_{out} (1 - s C_{gdp} / g_{mp})}{1 + bs + as^2}$$

$$R_{OUT} = r_{dsp} || R_L || (R_{F1} + R_{F2})$$

$$a = (C_O + C_{gdp}) R_{OUT} + (C_1 + C_{gdp}) R_{OEA} + g_{mp} R_{OUT} R_{OEA} C_{gdp}$$

$$b = R_{OEA} R_{OUT} (C_1 C_{gdp} + C_1 C_O + C_O C_{gdp})$$


Approximate Pole Zero Locations

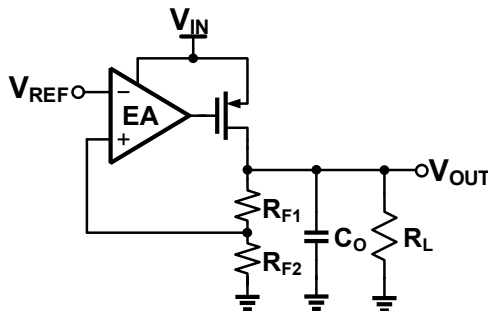

$$\omega_{PL} \approx \frac{1}{R_{OUT} \cdot C_O}$$


$$\omega_{PH} \approx \frac{1}{R_{OEA} \cdot [C_1 + g_{mp} \cdot R_{OUT} \cdot C_{gdp}]}$$
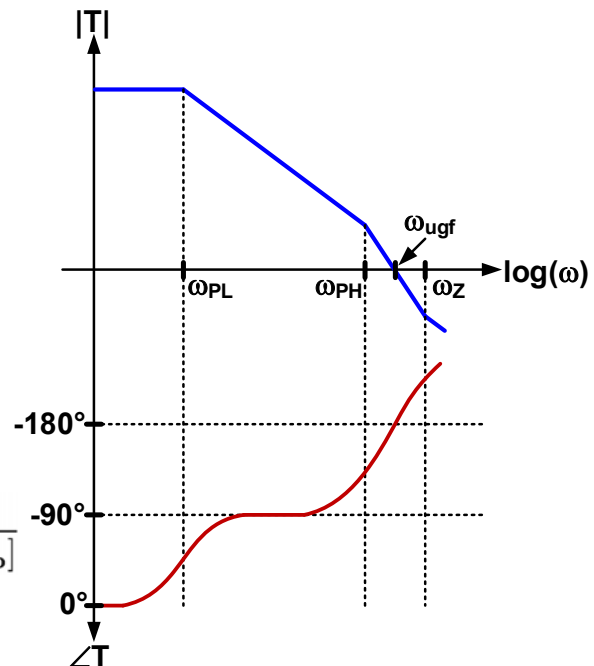
$$\omega_Z \approx \frac{g_{mp}}{C_{gdp}}$$



Frequency Compensation – I^[1]

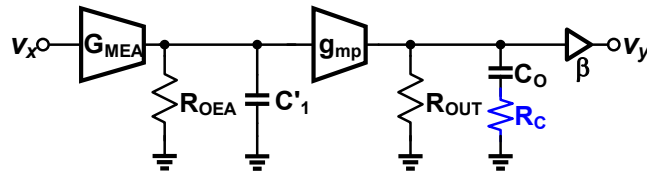- Introduce zero by adding series resistor R_C



$$Z_{out} = R_{OUT} \parallel \left(\frac{1}{sC_O} + R_C \right)$$

$$= \frac{(1 + sR_C C_O) \cdot R_{OUT}}{1 + s(R_{OUT} + R_C) \cdot C_O}$$


$$T(s) = \frac{\beta \cdot G_{MEA} \cdot R_{OEA} \cdot g_{mp} \cdot R_{OUT} \cdot (1 + s/\omega_Z)}{(1 + s/\omega_{PH}) (1 + s/\omega_{PL})}$$

Loop Gain Bode Plot (Compensated)

$$\omega_Z = \frac{1}{R_C \cdot C_O}$$


$$\omega_{PH} = \frac{1}{R_{OEA} \cdot C'_1}$$
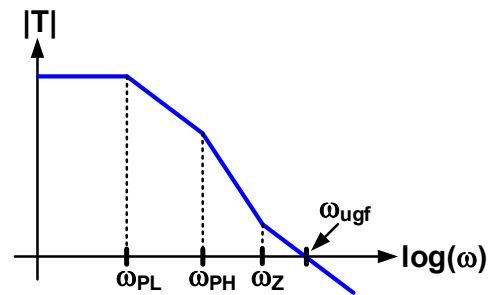
$$\omega_{PL} = \frac{1}{(R_{OUT} + R_C) \cdot C_O}$$



$$\Phi_M \approx \arctan \left(\frac{\omega_{ugf}}{\omega_Z} \right)$$

Typical LDO Implementation

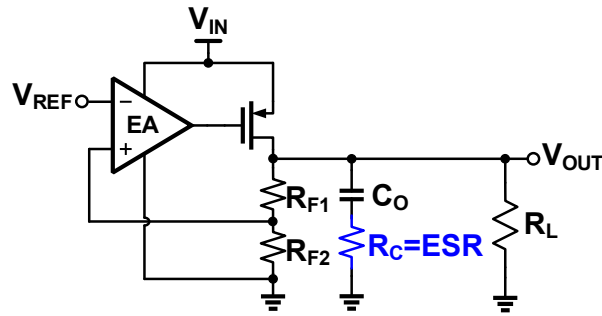


- ❑ Choose C_O and R_{ESR} to achieve desired phase margin
- ❑ Vendors specify min. R_{ESR} and C_O for stable operation

Can we introduce zero without using ESR resistance?

Frequency Compensation – II [2]

 - ❑ Introduce zero by adding **feed-forward capacitor**




$$\frac{V_X(s)}{V_{OUT}(s)} = \left(\frac{R_{F2}}{R_{F1} + R_{F2}} \right) \cdot \left(\frac{1 + sC_{F1}R_{F1}}{1 + sC_{F1}(R_{F1} || R_{F2})} \right)$$

$$\omega_{ZF} = \frac{1}{R_{F1}C_{F1}}$$

$$\omega_{PF} = \frac{1}{(R_{F1} || R_{F2})C_{F1}}$$

$$\frac{\omega_{PF}}{\omega_{ZF}} = 1 + \frac{R_{F1}}{R_{F2}} = \frac{V_{OUT}}{V_{REF}}$$


How to Eliminate ω_{PF}

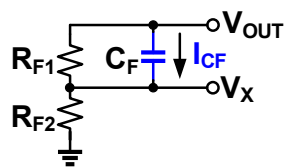

$$(V_{OUT} - V_X)(sC_F + 1/R_{F1}) = V_X/R_{F2}$$

$$V_{OUT}(sC_F + 1/R_{F1}) = V_X(1/R_{F1} + 1/R_{F2} + sC_F)$$

How to Eliminate ω_{PF}

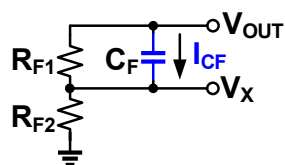


$$(V_{OUT} - V_X)(sC_F + 1/R_{F1}) = V_X/R_{F2}$$


$$V_{OUT}(sC_F + 1/R_{F1}) = V_X(1/R_{F1} + 1/R_{F2} + sC_F)$$




$$I_{CF} = (V_{OUT} - V_X)(sC_F)$$

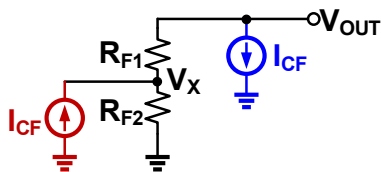


How to Eliminate ω_{PF}

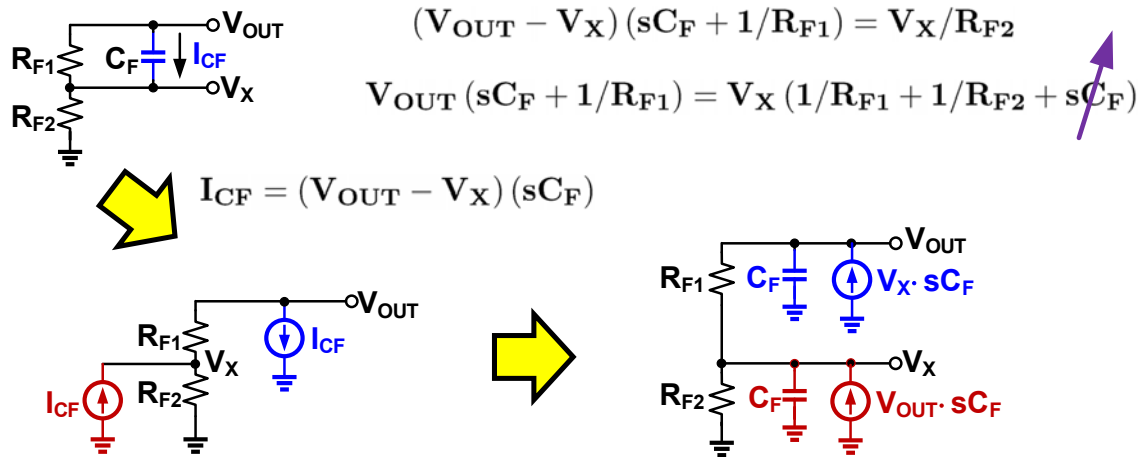

How to Eliminate ω_{PF}

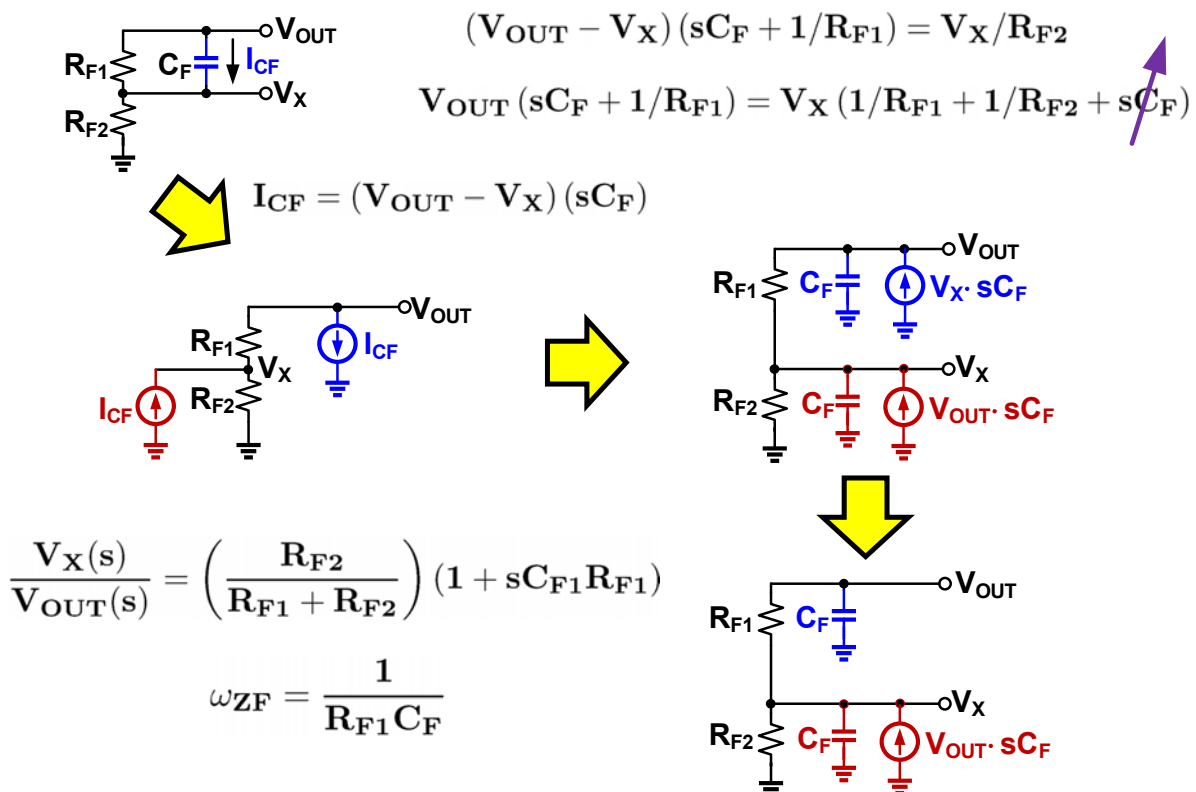

Frequency Comp. – II Implementation

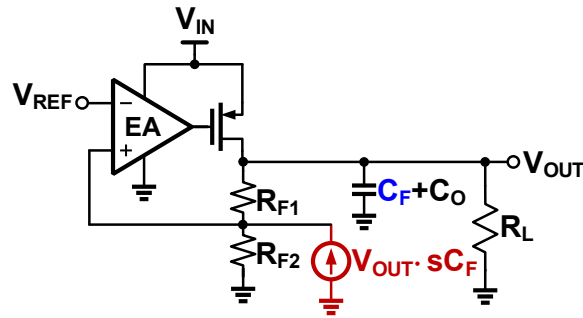


$$\omega_{PL} = \frac{1}{R_{OUT} \left(C_O - \frac{C_F}{\beta} \right)}$$

$$\omega_{PH} = \frac{1}{R_{OEA} [C_1 + g_{mp} R_{OUT} C_{gdp}]} \quad (\text{same as before})$$


$$\omega_{ZF} = \frac{1}{R_{F1} C_F}$$

$$\omega_{ZF} \sim \omega_{PH} < \omega_{UGF}$$

VCCS Implementation

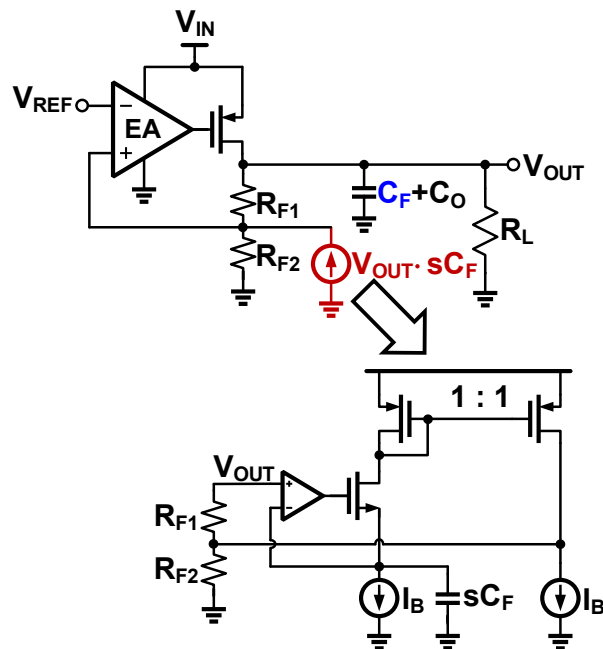


Frequency Compensation – III

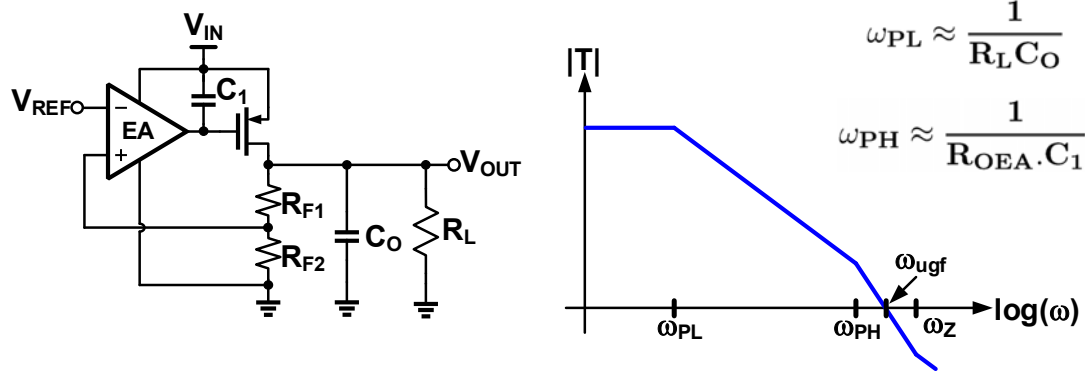

- ❑ Make $\omega_{PH} > \omega_{ugf}$
- ❑ Reducing C_1 is difficult
 - C_1 is set by I_{LOAD} and V_{DSAT} of pass device
- ❑ Reducing R_{OEA} degrades load/line regulation

Frequency Compensation – III [3]

 - ❑ Shield C_1 from loading EA using a [buffer](#)



$$\omega_{PL} = \frac{1}{R_L C_O}$$


$$\omega_{PH} = \frac{1}{R_{OEA} \cdot C_x}$$

$$C_x = C_{OEA} + C_{IBUF} \ll C_1$$

$$\omega_{PB} = \frac{1}{R_B \cdot C_1}$$

$$R_B \ll R_{OEA}$$


Buffer Implementation

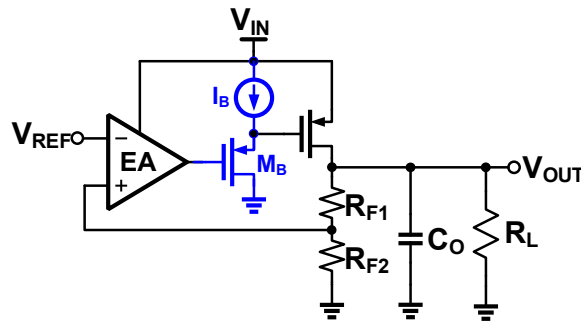

$$R_B \approx 1/g_{mB} \propto \frac{1}{(W/L)I_B}$$

- ❑ Source follower as a buffer
 - Small input capacitance
 - Lower output impedance → large power
- ❑ Use feedback to lower output impedance

Improved Buffer

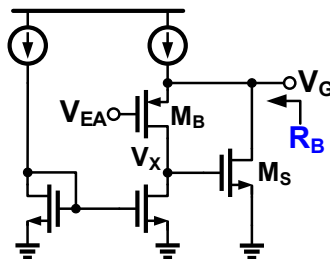


$$R_B \approx \frac{1}{(g_{mB} \cdot R_x) \cdot g_{mS}}$$

$$= \frac{1}{g_{mB} \cdot (g_{mS} \cdot R_x)}$$

- ❑ Shunt feedback reduces output impedance
 - Reduction factor proportional to loop gain
- ❑ Low power

Cap-less LDO

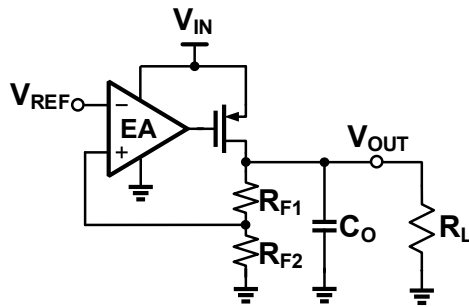


$$\omega_{P1} = \omega_{PL} = \frac{1}{R_{OEA} \cdot (C_1 + g_{mp} \cdot R_{OUT} \cdot C_{gdp})}$$

$$\omega_{P2} = \omega_{PH} = \frac{1}{R_{OUT} \cdot C_O}$$

$$\omega_Z = \frac{g_{mp}}{C_{gdp}}$$


- ❑ C_O less than few hundred pF
 - Difficult to make output pole dominant
- ❑ Need to make EA output pole dominant
 - Miller compensation
 - Cascode compensation

Miller Compensation

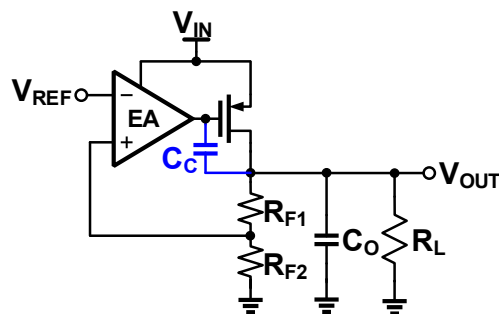


- ❑ Stability is compromised at large cap loads
 - Need large compensation capacitor ($C_O < 5C_C$)
 - Sensitive to load current variation
- ❑ Poor high frequency PSR

Cascode Compensation^[4]

 

- ❑ Suppresses feed-forward path
 - Moves RHP zero to a very high frequency
- ❑ Preserves Miller multiplication of C_C
- ❑ Pushes second pole to even higher frequencies

Cascode Compensation: Intuition

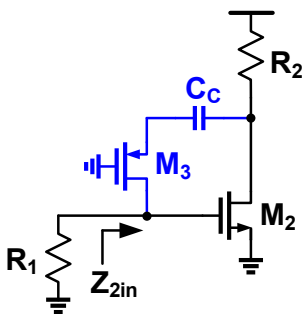


$$I_T = [V_T - (-g_{m2}R_2V_T)] C_C s$$

$$Z_{2in} = \frac{V_T}{I_T} = \frac{1}{(1 + g_{m2}R_2) C_C s}$$

$$\Rightarrow \omega_{p1} \approx \frac{1}{R_1 g_{m2} R_2 C_C}$$


Cascode Compensation: Intuition

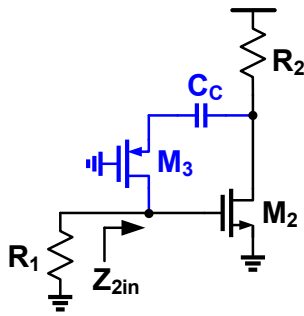

$$I_T = [V_T - (-g_{m2}R_2V_T)] C_{CS}$$

$$Z_{2in} = \frac{V_T}{I_T} = \frac{1}{(1 + g_{m2}R_2) C_C}$$

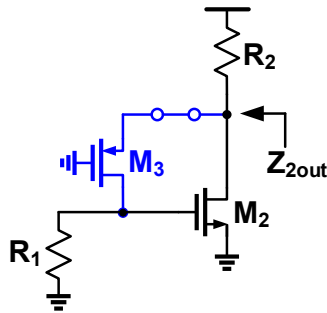
$$\Rightarrow \omega_{p1} \approx \frac{1}{R_1 g_{m2} R_2 C_C}$$



$$I_T = g_{m2}(g_{m3}R_1)V_T + \frac{V_T}{R_2}$$

$$\Rightarrow \omega_{p2} \approx \frac{g_{m2}(g_{m3}R_1)}{C_2}$$

LDO w/ Cascode Compensation

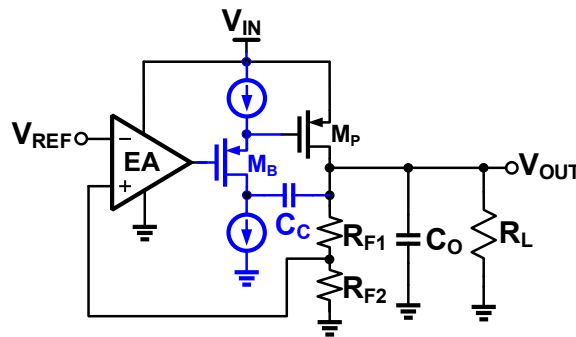


$$T(s) = \frac{\beta \cdot g_{mEA} \cdot g_{mp} \cdot R_{OE} \cdot R_{OUT}}{1 + s(R_{OE} \cdot C_1 + R_{OUT} \cdot C_C + R_{OUT} \cdot C_O + g_{mEA} \cdot R_{OUT} \cdot R_{OE} \cdot C_C) + s^2 R_{OE} \cdot R_{OUT} \cdot C_1 (C_C + C_O)}$$

$$p_1 \approx \frac{1}{(R_{OE} C_1 + R_{OUT} (C_C + C_O) + g_{mp} R_{OE} R_{OUT} C_C)}$$

$$p_2 \approx \frac{R_{OE} C_1 + R_{OUT} (C_C + C_O) + g_{mp} R_{OE} R_{OUT} C_C}{R_{OE} \cdot R_{OUT} \cdot C_1 (C_C + C_O)}$$

Cascode Compensation^[5]

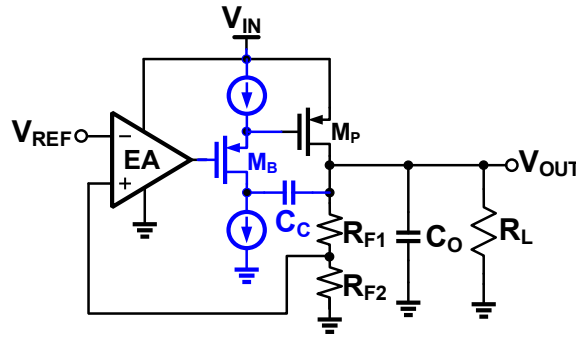

$$p_1 \approx \frac{1}{(R_{OE A} C_1 + R_{OUT} (C_C + C_O) + g_{mp} R_{OE A} R_{OUT} C_C)}$$


$$p_2 \approx \frac{R_{OE A} C_1 + R_{OUT} (C_C + C_O) + g_{mp} R_{OE A} R_{OUT} C_C}{R_{OE A} \cdot R_{OUT} \cdot C_1 (C_C + C_O)}$$

For small C_O

$$p_1 \approx \frac{1}{g_{mp} R_{OE A} R_{OUT} C_C}$$

$$p_2 \approx \frac{g_{mp} C_C}{C_1 (C_C + C_O)}$$

Cascode Compensation^[5]

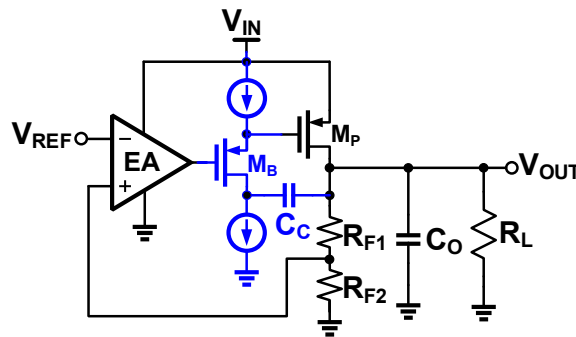

$$p_1 \approx \frac{1}{(R_{OE A} C_1 + R_{OUT} (C_C + C_O) + g_{mp} R_{OE A} R_{OUT} C_C)}$$

$$p_2 \approx \frac{R_{OE A} C_1 + R_{OUT} (C_C + C_O) + g_{mp} R_{OE A} R_{OUT} C_C}{R_{OE A} \cdot R_{OUT} \cdot C_1 (C_C + C_O)}$$


For large C_O

$$p_1 \approx \frac{1}{R_{OUT} (C_C + C_O)} \quad p_2 \approx \frac{1}{R_{OE A} C_1}$$

Stability Quality Factor


$$S \equiv p_2 / \omega_{UGF} \quad \frac{\partial S}{\partial C_O} = 0 \Rightarrow C_O^* \approx (g_{mp} R_1 - 1) C_C$$
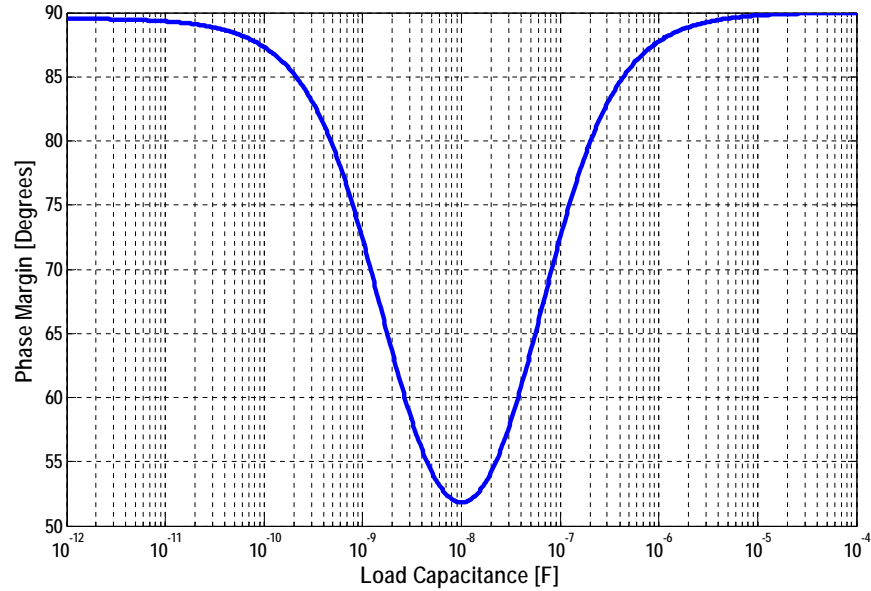
$$S_{MIN} = \frac{4}{g_{m1} R_1} \cdot \left(\frac{C_C}{C_1} \right) \Rightarrow \uparrow C_C \text{ or } \downarrow C_1$$




Phase Margin Vs. I_L [3]
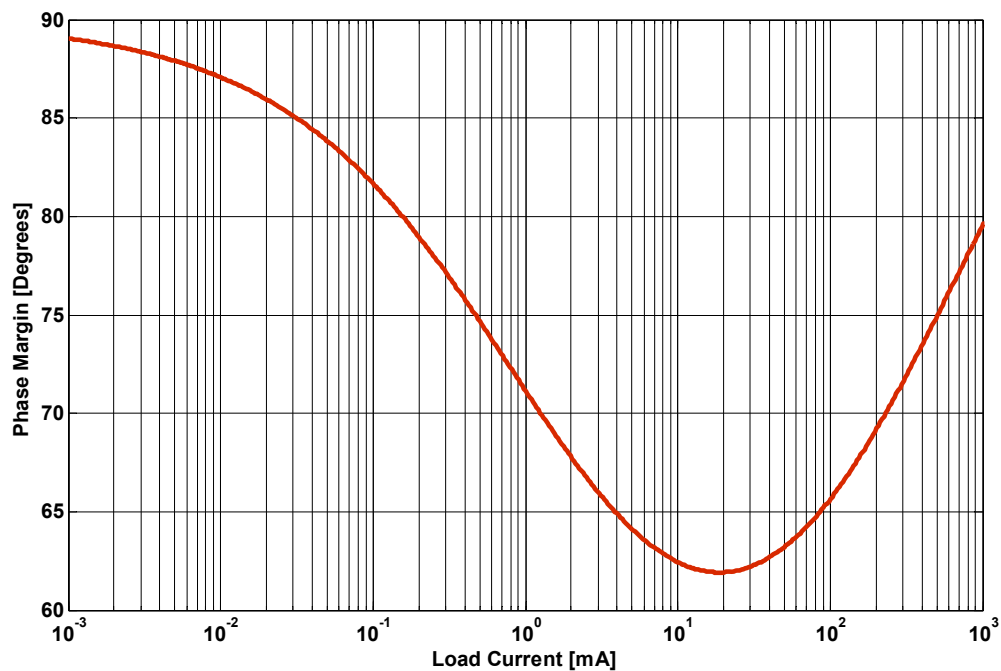
$$\frac{\partial S}{\partial g_{mp}} = \frac{4}{g_{m1} R_1} \frac{C_C}{C_1}$$




Power Supply Rejection

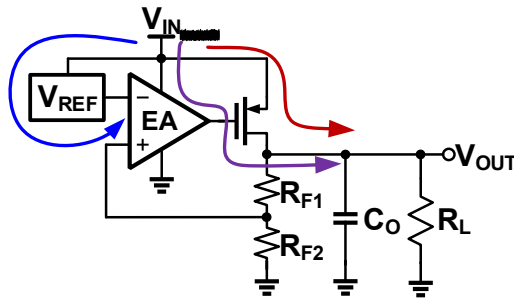


- ❑ Many paths from input to output
 - Reference generator
 - Error amplifier
 - Pass device
- ❑ Need to evaluate their combined effect on PSR

PSR Calculation

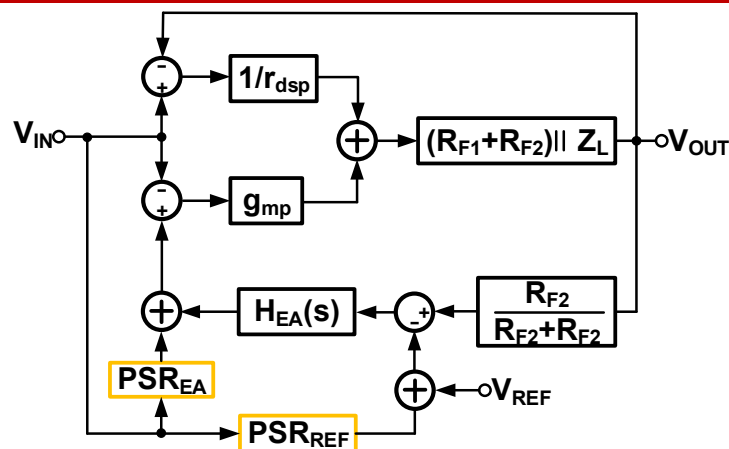

- ❑ PSR_{EA} = PSR of error amplifier
- ❑ PSR_{REF} = PSR of reference generator
- ❑ Signal flow analysis to determine overall PSR

PSR Calculation

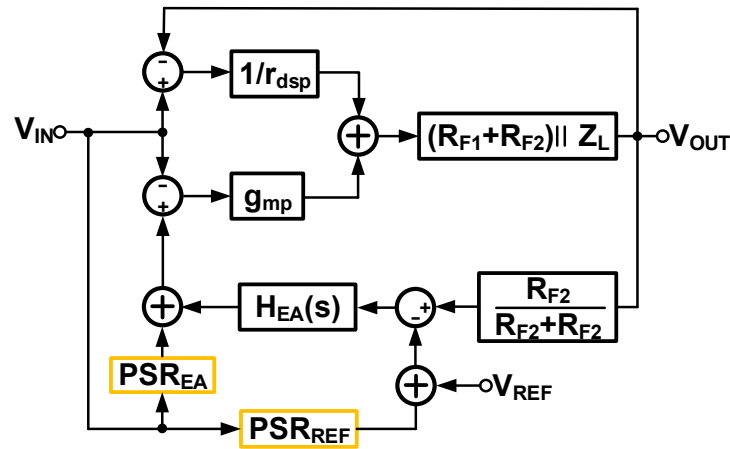


$$\left. \frac{V_{OUT}}{V_{IN}} \right|_{\text{pass}} = \frac{\left(g_{mp} + \frac{1}{r_{dsp}} \right) [(R_{F1} + R_{F2}) || Z_L]}{1 + g_{mp} [(R_{F1} + R_{F2}) || Z_L] \cdot \beta \cdot H_{EA}(s) + \frac{1}{r_{dsp}} [(R_{F1} + R_{F2}) || Z_L]}$$

$$\left. \frac{V_{OUT}}{V_{IN}} \right|_{EA} = \frac{-PSR_{EA} \cdot g_{mp} \cdot [(R_{F1} + R_{F2}) || Z_L]}{D(s)}$$

$$\left. \frac{V_{OUT}}{V_{IN}} \right|_{REF} = \frac{PSR_{REF} \cdot H_{EA}(s) \cdot g_{mp} \cdot [(R_{F1} + R_{F2}) || Z_L]}{D(s)}$$

Reducing Noise Leakage from Reference

 


$$\left. \frac{V_{OUT}}{V_{IN}} \right|_{REF} = \frac{PSR_{REF} \cdot H_{EA}(s) \cdot g_{mp} \cdot [(R_{F1} + R_{F2}) || Z_L]}{D(s)}$$

❑ PSR_{REF} sees low pass response

❑ Noise leakage improved by using a low pass filter

Error Amplifier PSR (Type – A)

□ PSR_{EA} depends on amplifier topology

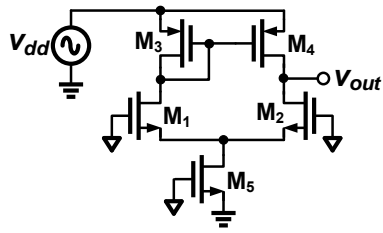


$$\frac{V_{\text{out}}}{V_{\text{dd}}} = -G_M \cdot R_{\text{out}}$$

$$R_{\text{out}} = (r_{\text{ds}2} || r_{\text{ds}4})$$


Error Amplifier PSR (Type – A)

□ PSR_{EA} depends on amplifier topology

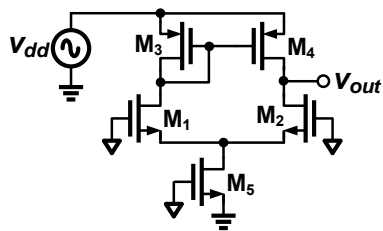

$$\frac{V_{\text{out}}}{V_{\text{dd}}} = -G_M \cdot R_{\text{out}}$$

$$R_{\text{out}} = (r_{\text{ds}2} || r_{\text{ds}4})$$

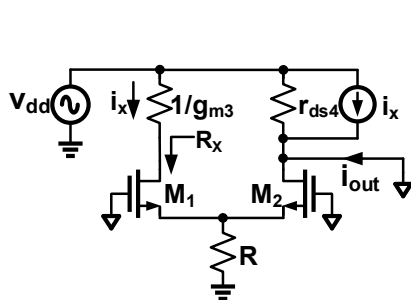

$$i_{\text{out}} = 2i_x + \frac{V_{\text{dd}}}{r_{\text{ds}4}}$$


$$R_x \approx g_{m1} \cdot r_{\text{ds}1} \cdot \frac{1}{g_{m2}} + r_{\text{ds}2} \simeq 2r_{\text{ds}1}$$

$$i_x = \frac{V_{\text{dd}}}{1/g_{m3} + 2r_{\text{ds}1}} \approx \frac{V_{\text{dd}}}{2r_{\text{ds}1}}$$

$$\Rightarrow G_M = r_{\text{ds}1} || r_{\text{ds}4}$$

Error Amplifier PSR (Type – A)


❑ PSR_{EA} depends on amplifier topology

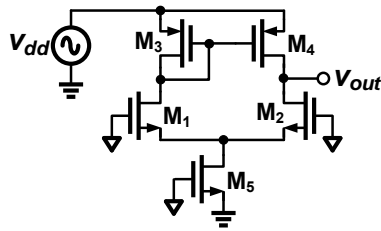

$$\frac{V_{\text{out}}}{V_{\text{dd}}} = -G_M \cdot R_{\text{out}}$$

$$R_{\text{out}} = (r_{\text{ds}2} \parallel r_{\text{ds}4})$$
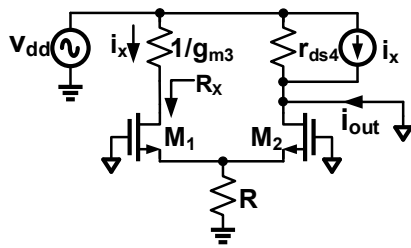
$$\frac{V_{\text{out}}}{V_{\text{dd}}} \approx 1$$




$$i_{\text{out}} = 2i_x + \frac{V_{\text{dd}}}{r_{\text{ds}4}}$$

$$R_x \approx g_{\text{m}1} \cdot r_{\text{ds}1} \cdot \frac{1}{g_{\text{m}2}} + r_{\text{ds}2} \simeq 2r_{\text{ds}1}$$

$$i_x = \frac{V_{\text{dd}}}{1/g_{\text{m}3} + 2r_{\text{ds}1}} \approx \frac{V_{\text{dd}}}{2r_{\text{ds}1}}$$

$$\Rightarrow G_M = r_{\text{ds}1} \parallel r_{\text{ds}4}$$

Error Amplifier PSR (Type – B)

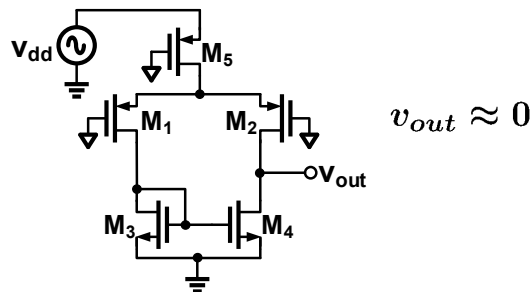

$$v_{\text{out}} \approx 0$$


❑ None of the supply-noise appears at the output

■ $\text{PSR} = \infty$

❑ Good for regulator with NMOS output stage

■ Prevents noise leakage through NMOS gate

PMOS Output Stage PSR

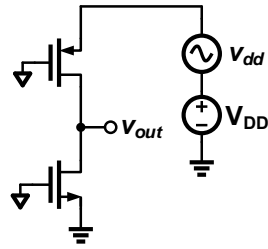


$$\frac{v_{out}(s)}{v_{dd}(s)} \approx g_{m1} (r_{ds1} || R_L)$$


□ Two scenarios for PSR calculation

1. Gate of M_1 **not coupled to V_{DD}**
 - Behaves as a common gate stage

PMOS Output Stage PSR

 

$$\frac{v_{out}(s)}{v_{dd}(s)} \approx g_{m1} (r_{ds1} || R_L)$$

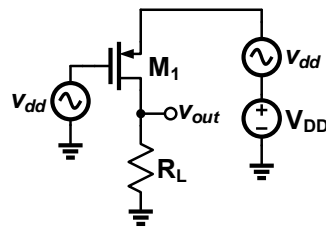


$$\frac{v_{out}(s)}{v_{dd}(s)} = \frac{R_L}{r_{ds1} + R_L}$$


□ Two scenarios for PSR calculation

1. Gate of M_1 **not coupled to V_{DD}**
 - Behaves as a common gate stage
2. Gate of M_1 **tightly coupled to V_{DD}**
 - Becomes a resistor divider

NMOS Output Stage PSR

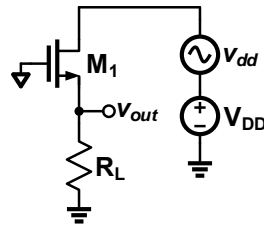

$$\frac{V_{out}(s)}{V_{dd}(s)} = \frac{1}{r_{ds1}} \left(\frac{1}{g_{mn1} || r_{ds1} || R_L} \right) \approx \frac{1}{g_{m1} r_{ds1}}$$

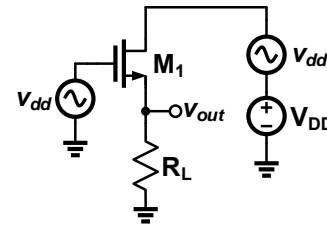

$$\frac{V_{out}(s)}{V_{dd}(s)} \approx 1$$

□ Two scenarios for PSR calculation



1. Gate of M_1 **not coupled to V_{DD}**
 - M_1 acts as a cascode
2. Gate of M_1 **tightly coupled to V_{DD}**
 - Behaves as a source follower

Error Amp. and Output Stage Possibilities^[6]



□ Four possibilities

1. NMOS amplifier & PMOS output stage
2. NMOS amplifier & NMOS output stage
3. PMOS amplifier & PMOS output stage
4. PMOS amplifier & NMOS output stage

□ Cases (1) and (4) yield **best PSR**

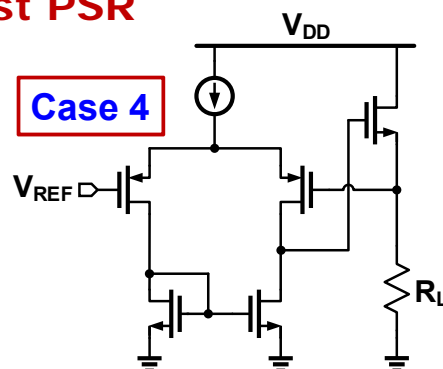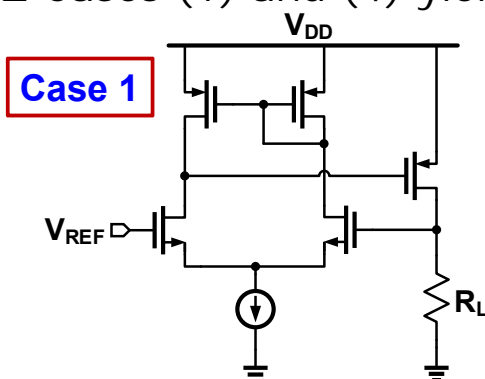

Regulator PSR_{1/2}

 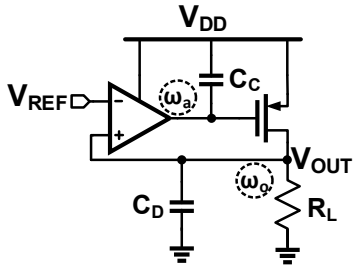

$$\omega_a = \frac{1}{r_{oa} C_C}$$

$$\omega_o = \frac{1}{(r_{dsP} \parallel R_L) C_D}$$

$$A_a = g_{ma} r_{oa}$$



$$A_o = g_{mP} (r_{dsP} \parallel r_{vco})$$

$$S_{V_{dd}} = \frac{R_L}{R_L + r_{dsP}}$$

$$\frac{v_{out}(s)}{v_{dd}(s)} = \frac{S_{V_{dd}} \left(1 + \frac{s}{\omega_a}\right)}{\left(1 + \frac{s}{\omega_a}\right) \left(1 + \frac{s}{\omega_o}\right) + A_a A_o}$$

$$\frac{v_{out}(s)}{v_{dd}(s)} = \frac{S_{V_{dd}}}{\left(1 + \frac{s}{\omega_o}\right) (1 + LG(s))}$$

Regulator PSR_{2/2}

 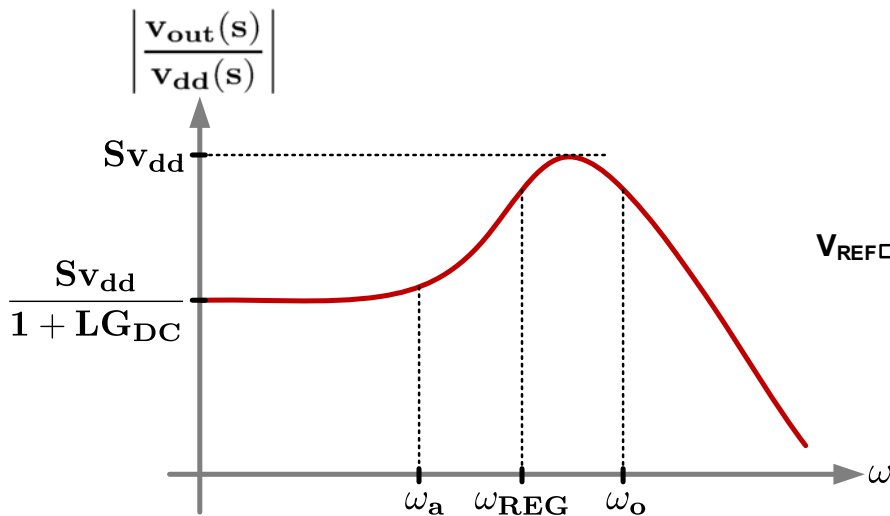


$$\frac{v_{out}(s)}{v_{dd}(s)} = \frac{S_{V_{dd}} \left(1 + \frac{s}{\omega_a}\right)}{\left(1 + \frac{s}{\omega_a}\right) \left(1 + \frac{s}{\omega_o}\right) + A_a A_o}$$

PSR Improvement Techniques


1. NMOS output stage
2. Make regulator output pole dominant
3. Cascaded regulators
4. Replica regulators

NMOS Output Stage LDO

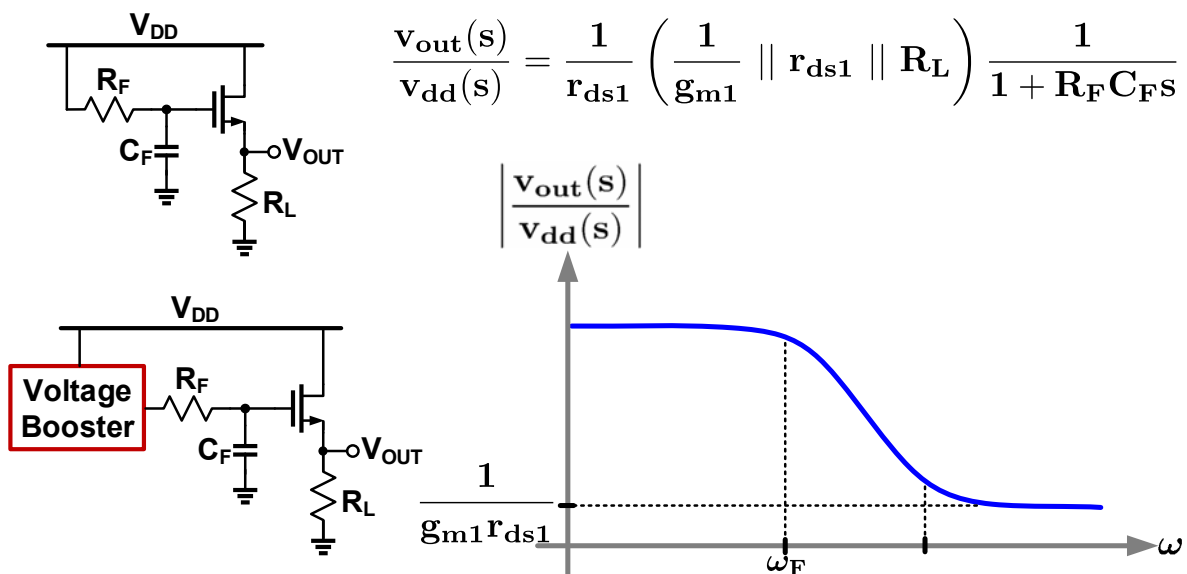


- ❑ Large dropout voltage
- ❑ Poor low frequency PSR

PMOS LDO w/ Output Pole Dominant

 


- ❑ No peaking in the supply noise transfer curve
 - Superior supply noise rejection
- ❑ Needs very large capacitors: C_C and C_D

Cascaded LDOs

 


- ❑ Dropout voltage traded for PSR
- ❑ Co-optimize the regulators for best PSR

Replica-based LDO^{[7],[8]}

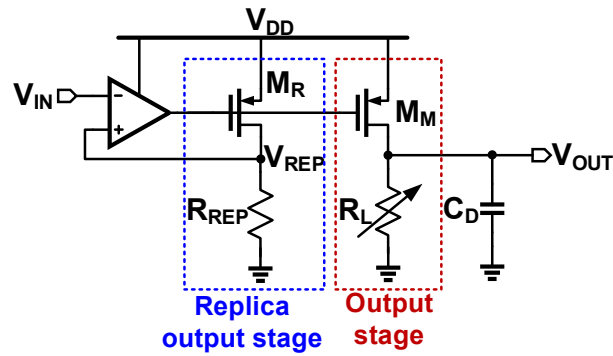

- Indirect output regulation
 - Only scaled replica output is regulated
 - Accuracy depends on matching
- Stability independent of the load
 - Variable load outside the feedback loop
- Exhibits superior PSR performance

Replica-based LDO PSR_{1/2}

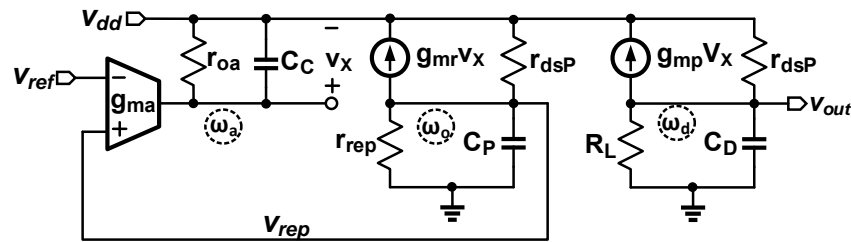


$$S_M = \frac{R_L}{R_L + r_{dsM}}$$

$$\frac{v_{out}(s)}{v_{dd}(s)} = \frac{S_M \left(1 + \frac{s}{\omega_a}\right) \left(1 + \frac{s}{\omega_o}\right)}{\left(1 + \frac{s}{\omega_d}\right) \left[\left(1 + \frac{s}{\omega_a}\right) \left(1 + \frac{s}{\omega_o}\right) + A_a A_o \right]}$$

$$\frac{v_{out}(s)}{v_{dd}(s)} = \frac{S_M}{\left(1 + \frac{s}{\omega_d}\right) (1 + LG(s))}$$

Replica-based LDO PSR_{2/2}

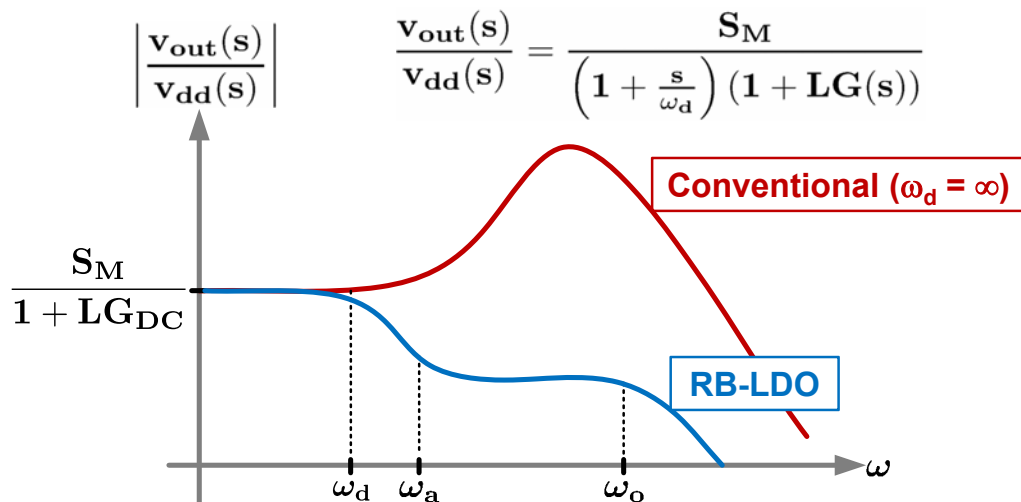

❑ Large PSR improvement beyond ω_d

❑ $\omega_d > \omega_a$ eliminates "peaking"

References

1. *ESR, Stability, and the LDO Regulator*, 2002 : Texas Instruments.
2. C. Chava and J. Silva-Martinez "A robust frequency compensation scheme for LDO voltage regulators", *IEEE Trans. Circuits Syst. I, Reg. Papers*, vol. 51, no. 6, pp. 1041-1050 2004.
3. M. Al-Shyoukh, H. Lee, R. Perez, "A transient-enhanced low-quiescent current low-dropout regulator with buffer impedance attenuation", *IEEE J. Solid-State Circuits*, pp. 1732-1742 vol. 42, Aug. 2007.
4. B. K. Ahuja, "An improved frequency compensation technique for CMOS operational amplifiers", *IEEE J. Solid-State Circuits*, vol. SC-18, no. 6, pp.629 -633 1983.
5. R. Reay and G. Kovas, "An unconditionally stable two-stage CMOS amplifier", *IEEE J. Solid-State Circuits*, vol. 30, pp.591 -594 1995
6. V. Gupta , G. Rincon-Mora and P. Raha "Analysis and design of monolithic, high PSR, linear regulators for SoC applications", *Proc. IEEE Int. Syst. Chip Conf.*, pp.311 -315 2004.
7. G. W. den Besten and B. Nauta, "Embedded 5-V-to-3.3-V voltage regulator for supplying digital ICs in 3.3 V technology", *IEEE J. Solid-State Circuits*, vol. 33, no. 7, pp.956 -962 1998.
8. A. Arakali, S. Gondi, and P. Hanumolu, "Low-power supply-regulation techniques for ring oscillators in phase-locked loops using a split-tuned architecture," *IEEE J. Solid-State Circuits*, vol. 44, no. 8, pp. 2169-2181, Aug. 2009.

Acknowledgments

- ❑ Mrunmay Talegoankar, Saurabh Saxena, Seong-Joong Kim, Tianyu Wang, and Ahmed Elkholy for reviewing, providing detailed feedback and for assistance with preparation

- ❑ Eric Naviasky for coordination